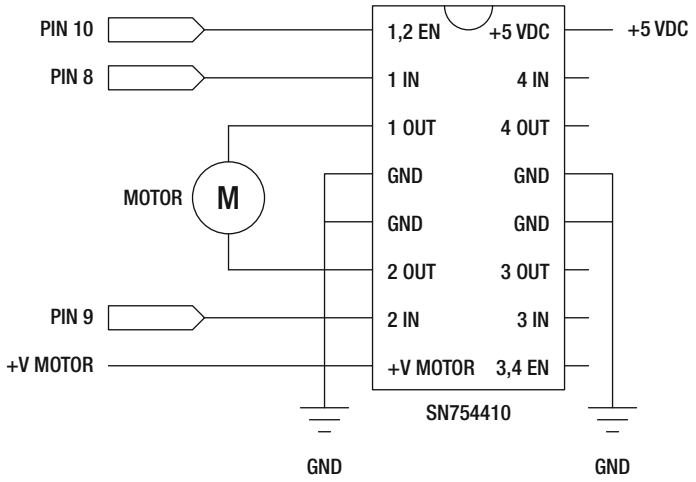


Figure 11-6. *H-Bridge and DC Motor schematic*

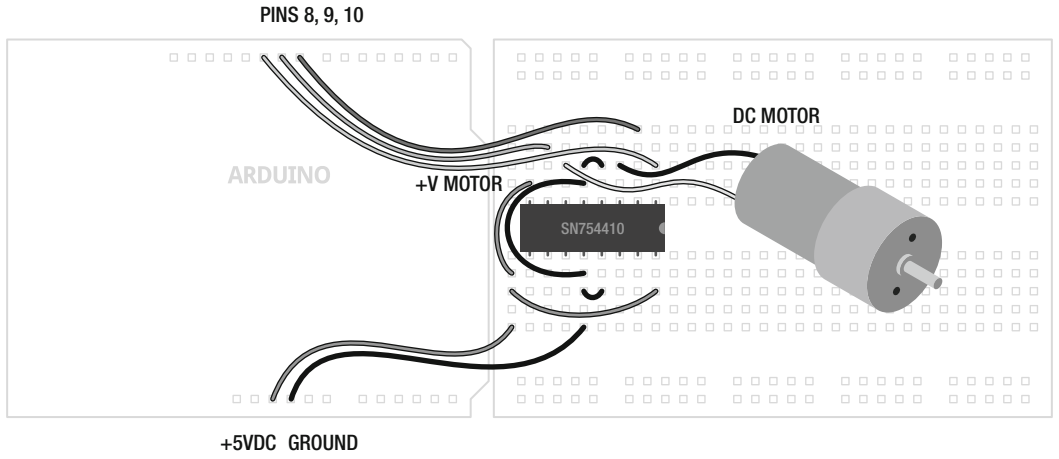


Figure 11-7. *H-Bridge and DC Motor illustration*

When configured as shown, pins 8 and 9 will control the direction of the motor using digital outputs and the `digitalWrite()` function, while pin 10 will control the motor's speed using `analogWrite()` with 0 being off and 255 being full speed ahead. To get a sense of how these two pins control the direction of the motor, see Table 11-1.