Hooking It Up

For this project, we are adding a simple circuit for the tilt switch (or other type of mechanical switch) to work as a very basic sensor. In this circuit, when the switch is open, a resistor connects the input pin to ground, providing a `LOW` signal. When the switch is closed it creates a connection to +5v, providing a `HIGH` signal. We will use these two states to light up our LED. Figures 4-1 and 4-2 show how to wire it up.

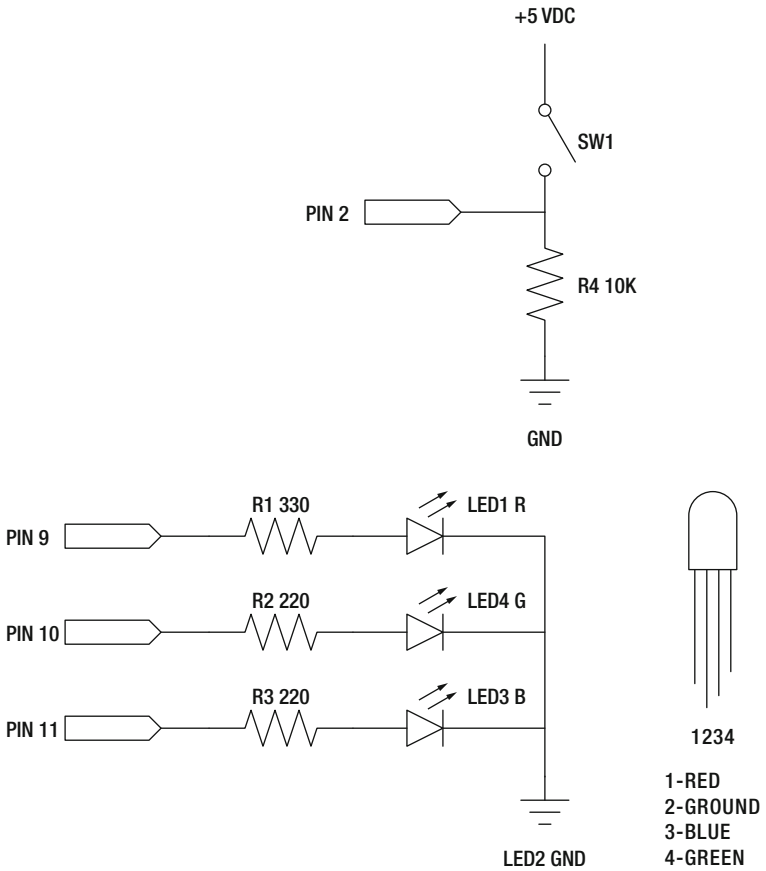


Figure 4-1. *Tilt Blink schematic*